



**University of
Nottingham**

UK | CHINA | MALAYSIA

Digital Blocks and ALU Design

Dr. Heng Yu

AY2023-24, Spring Semester
COMP1047: Systems and Architecture
Week 4



Today's outline

- ✓ Basic digital building blocks
 - Gates, Arithmetic circuits, multiplexers, registers
- ✓ Constructing an arithmetic logic unit
 - Add, sub, and, or, nor
 - Set-on-less-than






Learning Objectives

- Recap on basic digital circuit components
- Understand the function and control of a MIPS ALU
- Design a MIPS ALU with given arithmetic operations

Introduction


- Digital building blocks include:
 - ➔ Gates, arithmetic circuits, multiplexers, decoders, registers, counters, memory arrays, logic arrays, etc.
- Building blocks are important in their own right and they demonstrate hierarchy, modularity, and regularity:
 - ➔ They are built from a hierarchy of simpler components.
 - ➔ They have well-defined interfaces and functions.
 - ➔ Their regular structure is easily extended to different sizes.
- We'll use many of these building blocks to build a microprocessor in week 5.

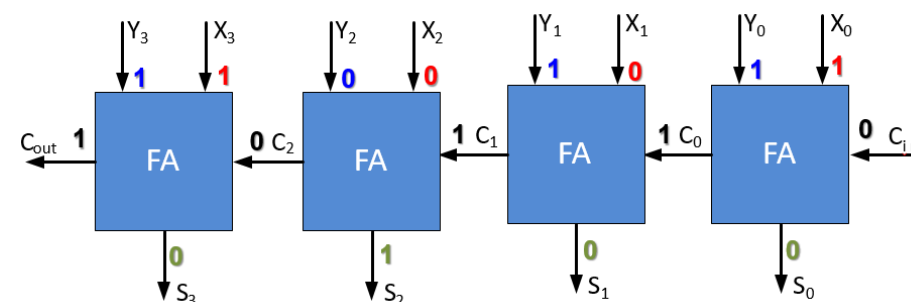  

Digital Building Blocks


1-bit adders

Half Adder

 

$S = A \oplus B$
 $C_{out} = AB$


Full Adder

 

$S = A \oplus B \oplus C_{in}$
 $C_{out} = AB + AC_{in} + BC_{in}$

Multi-bit adders

 - ✓ Also called carry propagate adder (CPA). Several types of design available:
 - ★ Ripple carry adder (slow)
 - ★ Carry-Lookahead adder
 - ★ Prefix adder
- ✓ Faster adders require more hardware.



General symbol of a multi-bit adder.

Ripple carry adder


- ✓ Chain 1-bit adders together
- ✓ Disadvantage: **slow**
- ✓ The delay of an N -bit ripple-carry adder is:

$$t_{\text{ripple}} = N t_{FA}$$

where t_{FA} is the delay of a full adder

Think about it:

Illustrate the process that a RCA works.

 


A 32-bit ripple carry adder.


Subtractor

- $-B = B' + 1$ (2's complement representation)
- $A - B = A + B' + 1$ (use CPA where $C_{in} = 1$)
- Bit-wise inverse of B is B'

Symbol

 


Implementation

 


Comparator: Equality


Symbol

 

Implementation

 

XNOR

 


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


Comparator: Less than

 - Calculate $A - B$. If $A < B$, then result is negative \Rightarrow 2's complement numbers, (N-1)th bit is 1.



Multiplexer

 - Selects between **one** of N inputs to connect to the output.
- $\log_2 N$ -bit input selection



S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		



Think about it:

for 4-input mux, how many S bits are required? How about 8, 16, 32, ...

A 2-to-1 multiplexer

Register

  - Register: stores data in a circuit
- Uses a clock signal to determine when to update the stored value
- Edge-triggered: update when Clk changes from 0 to 1 (rising edge)
- Synchronous circuit



Today's outline

- ✓ Basic digital building blocks
 - Gates, Arithmetic circuits, multiplexers, registers
- ✓ Constructing an arithmetic logic unit
 - Add, sub, and, or, nor
 - Set-on-less-than

Define our ISA first!

Let's use a *subset* of the MIPS instructions.

✓ R-Type:

- ★ `add rd, rs, rt`
- ★ `sub rd, rs, rt`
- ★ `and rd, rs, rt`
- ★ `or rd, rs, rt`
- ★ `slt rd, rs, rt`

✓ Load/Store:




- ★ `lw rt,rs,imm16`
- ★ `sw rt,rs,imm16`

✓ Imm operand:

- ★ `addi rt,rs,imm16`

✓ Branch:

- ★ `beq rs,rt,imm16`

   

Define our ISA first!

Let's use a *subset* of the MIPS instructions.

✓ R-Type:

- ★ `add rd, rs, rt`
- ★ `sub rd, rs, rt`
- ★ `and rd, rs, rt`
- ★ `or rd, rs, rt`
- ★ `slt rd, rs, rt`

✓ Load/Store:

- ★ `lw rt,rs,imm16`
- ★ `sw rt,rs,imm16`


✓ Imm operand:

- ★ `addi rt,rs,imm16`

✓ Branch:

- ★ `beq rs,rt,imm16`

 What are the common operations involved in those instructions?



Requirements: must support the following arithmetic and logic operations

add, sub: two's complement adder/subtractor


and, or : logical AND, logical OR

slt (set on less than): two's complement adder with inverter, check sign bit of result

Functional specification

Remember the operations needed:

add, sub, and, or, slt

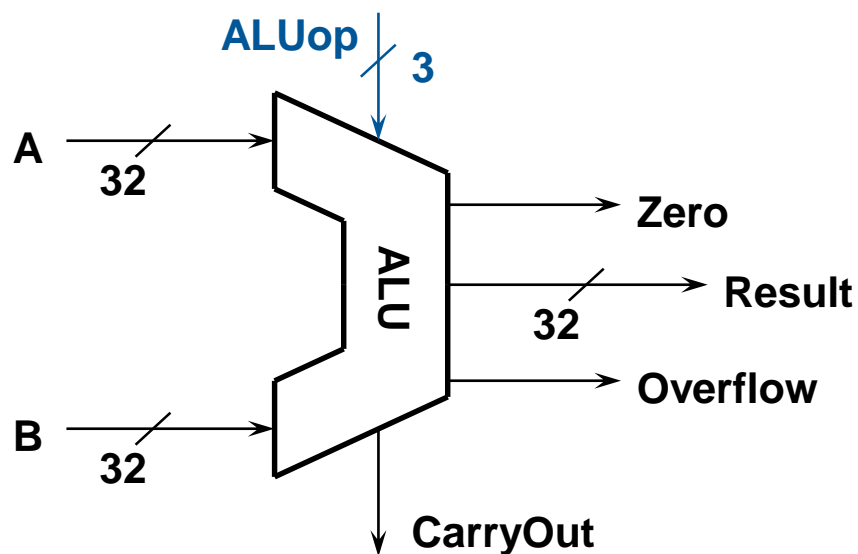

<u>ALU Control (ALUop)</u>	<u>Operation</u>
000	and
001	or
010	add
110	subtract
111	set-less-than





Why ALUop needs 3 bits?

A bit-slice ALU

➔ Design trick 1: **divide and conquer**

 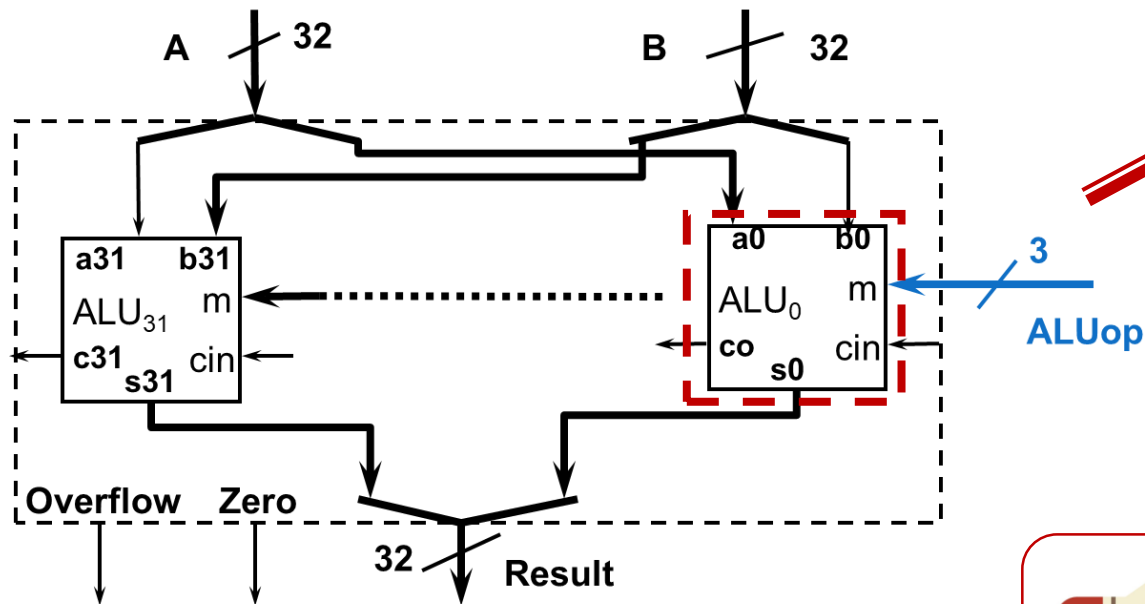
- Break the problem (32-bit ALU) into simpler problems (1-bit ALU), solve them and glue together the solution.



Note that the 'overflow' and 'zero' signals are not shown in this material, for simplicity. Basically, you need to design additional and specific circuits to output them. Take them as exercises with you.

A bit-slice ALU

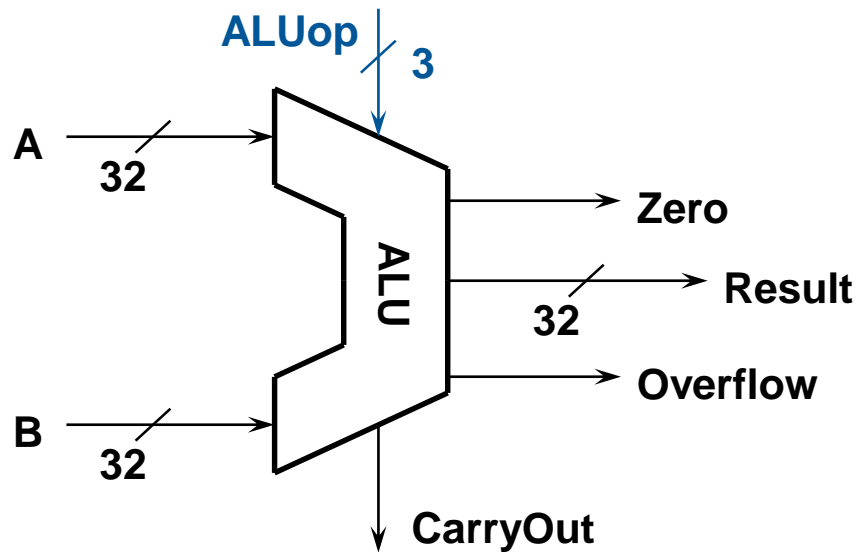- ➔ Design trick 2: [Work on what you already have](#)
- Solve part of the problem and extend based on it.
 - E.g., realize the 'and', 'or', and 'add' functionalities, then extend to 'sub', and 'slt'.



ALU Control (ALUOp)

000

001

010

110

111

Operation

and

or

add

subtract

set-less-than



Designing the ALU

- Let's make a pre-design analysis.
- What are the digital building blocks really needed to realize the five operations ('and', 'or', 'add', 'sub', and 'slt')?
 - One **AND** gate, one **OR** gate, and one **ADDER**.
 - 'sub' can be done by the **ADDER**.
 - 'slt' needs to subtract, so it can also be done by the **ADDER**.
 - One **multiplexer** for the ALUop control signal to select and output one result from the multiple incoming results (namely, from AND, OR, ADDER)
 - Maybe more.


<u>ALU Control (ALUop)</u>	<u>Operation</u>
000	and
001	or
010	add
110	subtract
111	set-less-than

Designing the ALU

- Let's design the 'slt' functionality.
- What does 'slt' do, and what does it output?
 - Firstly, 'slt Y, x1, x2' firstly subtracts x2 from x1 (i.e., $x1 - x2$)
 - Then, it should compare the result with zero.
 - If $x1 - x2 < 0$, then Y is set ($Y = 1$)
 - Else, then $Y = 0$.
 - Given Y being 32-bit binary
 - If $x1 - x2 < 0$, then Y is set ($Y = 0000 \dots 0001$)
 - Else, then $Y = 0000 \dots 0000$.

But how to make $Y = 1$ when $x1 - x2 < 0$?

 - In 2's complement format, the result of $x1 - x2$ is $1xxx \dots xxxx$, if $x1 - x2 < 0$. Only need to shift the leading digit back, from position 31 to position 0. This is how Y is obtained.




'slt' is a 'sub', but
needs special
attendance.






The ALU Design

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
110	$A - B$
111	SLT

Digital design and computer architecture,
1st or 2nd ed; by D. Harris & S. Harris

 - ✓ Available in UNNC library ([link](#))
- ✓ A simplified version of the Patterson & Hennessey Book.
- ✓ An ARM RISC ISA version also available in library.





University of
Nottingham

UK | CHINA | MALAYSIA

Stay Tuned.