

## COMP1036 Computer Fundamentals

### Lab 3

---

Below is a list of all the chip interfaces in the Hack chip-set. If you need to use a chip-part, you can copy-paste the chip interface and proceed to fill in the missing data. This is a very useful list to have bookmarked or printed.

```
Add16(a= ,b= ,out= );
ALU(x= ,y= ,zx= ,nx= ,zy= ,ny= ,f= ,no= ,out= ,zr= ,ng= );
And16(a= ,b= ,out= );
And(a= ,b= ,out= );
ARegister(in= ,load= ,out= );
Bit(in= ,load= ,out= );
CPU(inM= ,instruction= ,reset= ,outM= ,writeM= ,addressM= ,pc= );
DFF(in= ,out= );
DMux4Way(in= ,sel= ,a= ,b= ,c= ,d= );
DMux8Way(in= ,sel= ,a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= );
DMux(in= ,sel= ,a= ,b= );
DRegister(in= ,load= ,out= );
FullAdder(a= ,b= ,c= ,sum= ,carry= );
HalfAdder(a= ,b= ,sum= , carry= );
Inc16(in= ,out= );
Keyboard(out= );
Memory(in= ,load= ,address= ,out= );
Mux16(a= ,b= ,sel= ,out= );
Mux4Way16(a= ,b= ,c= ,d= ,sel= ,out= );
Mux8Way16(a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= ,sel= ,out= );
Mux(a= ,b= ,sel= ,out= );
Nand(a= ,b= ,out= );
Not16(in= ,out= );
Not(in= ,out= );
Or16(a= ,b= ,out= );
Or8Way(in= ,out= );
Or(a= ,b= ,out= );
PC(in= ,load= ,inc= ,reset= ,out= );
RAM16K(in= ,load= ,address= ,out= );
RAM4K(in= ,load= ,address= ,out= );
RAM512(in= ,load= ,address= ,out= );
RAM64(in= ,load= ,address= ,out= );
RAM8(in= ,load= ,address= ,out= );
Register(in= ,load= ,out= );
ROM32K(address= ,out= );
```

```
Screen(in= ,load= ,address= ,out= );  
Xor(a= ,b= ,out= );
```

1. Work out the representation for the following unsigned numbers by hand.

- (a) 45
- (b) 1026

### **Solution**

```
remainder  
45 / 2 1  
22 / 2 0  
11 / 2 1  
5 / 2 1  
2 / 2 0  
1 / 2 1  
0
```

The result is 101101

```
remainder  
1026 / 2 0  
513 / 2 1  
256 / 2 0  
128 / 2 0  
64 / 2 0  
32 / 2 0  
16 / 2 0  
8 / 2 0  
4 / 2 0  
2 / 2 0  
1 / 2 1  
0
```

The result is 10000000010

2. Work out the two's complement representations for the following signed numbers by hand(using 16-bits representation).

- (a) 26

### **Solution**

0000000000011010

(b) -130

**Solution**

```
130(decimal) = 0000000010000010(binary)
Take bit wise inverse = 1111111101111101
Add 1 = 1111111101111110
```

3. Implement the following circuits:

(a) HalfAdder

Half adder. Computes sum, the least significant bit of  $a + b$ , and carry, the most significant bit of  $a + b$ .

**Solution**

```
CHIP HalfAdder {
  IN a, b;    // 1-bit inputs
  OUT sum,    // Right bit of a + b
      carry;  // Left bit of a + b

  PARTS:
    Xor(a=a, b=b, out=sum);
    And(a=a, b=b, out=carry);
}
```

(b) FullAdder

Full adder. Computes sum, the least significant bit of  $a + b + c$ , and carry, the most significant bit of  $a + b + c$ .

**Solution**

```
CHIP FullAdder {
  IN a, b, c; // 1-bit inputs
  OUT sum,    // Right bit of a + b + c
      carry;  // Left bit of a + b + c

  PARTS:
    HalfAdder(a=a, b=b, sum=w1, carry=c1);
    HalfAdder(a=w1, b=c, sum=sum, carry=c2);
    Xor(a=c1, b=c2, out=carry);
}
```

(c) Add16

Adds two 16-bit values.  
The most-significant carry bit is ignored.

## Solution

```
CHIP Add16 {  
  IN a[16], b[16];  
  OUT out[16];
```

PARTS:

```
HalfAdder(a=a[0], b=b[0], sum=out[0], carry=carry1);  
FullAdder(a=a[1], b=b[1], c=carry1, sum=out[1], carry=carry2);  
FullAdder(a=a[2], b=b[2], c=carry2, sum=out[2], carry=carry3);  
FullAdder(a=a[3], b=b[3], c=carry3, sum=out[3], carry=carry4);  
FullAdder(a=a[4], b=b[4], c=carry4, sum=out[4], carry=carry5);  
FullAdder(a=a[5], b=b[5], c=carry5, sum=out[5], carry=carry6);  
FullAdder(a=a[6], b=b[6], c=carry6, sum=out[6], carry=carry7);  
FullAdder(a=a[7], b=b[7], c=carry7, sum=out[7], carry=carry8);  
FullAdder(a=a[8], b=b[8], c=carry8, sum=out[8], carry=carry9);  
FullAdder(a=a[9], b=b[9], c=carry9, sum=out[9], carry=carry10);  
FullAdder(a=a[10], b=b[10], c=carry10, sum=out[10], carry=carry11);  
FullAdder(a=a[11], b=b[11], c=carry11, sum=out[11], carry=carry12);  
FullAdder(a=a[12], b=b[12], c=carry12, sum=out[12], carry=carry13);  
FullAdder(a=a[13], b=b[13], c=carry13, sum=out[13], carry=carry14);  
FullAdder(a=a[14], b=b[14], c=carry14, sum=out[14], carry=carry15);  
FullAdder(a=a[15], b=b[15], c=carry15, sum=out[15], carry=carry16);
```

```
}
```