


Revision – Part 1

Dr Tianxiang Cui


Boolean Logic

Elementary Logic Gates

$$A = \bar{A}$$

 

$$A \text{ AND } B = A \cdot B$$

 


$$A \text{ OR } B = A + B$$



$$A \text{ XOR } B = A \oplus B$$


 
$$A \text{ NAND } B = \overline{A \cdot B}$$



$$A \text{ NOR } B = \overline{A + B}$$



Collection of Elementary Logic Gates

$$A = \bar{A} \quad \text{---} \triangle \text{---}$$

A	\bar{A}
0	1

$$A \text{ XOR } B = A \oplus B \quad \text{---} \text{---} \text{---} \text{---} \text{---}$$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$$A \text{ AND } B = A \cdot B \quad \text{---} \text{---} \text{---} \text{---}$$

A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

$$A \text{ NAND } B = \overline{A \cdot B} \quad \text{---} \text{---} \text{---} \text{---} \text{---}$$

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

$$A \text{ OR } B = A + B \quad \text{---} \text{---} \text{---} \text{---}$$

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

$$A \text{ NOR } B = \overline{A + B} \quad \text{---} \text{---} \text{---} \text{---} \text{---}$$

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Logic

All chips constructed from elementary logic gates

- Every chip can be built from a combination of:
 - AND
 - OR
 - NOT
 - No integration, division, differentiation...
 - “**Canonical Representation**”
- AND, OR and NOT can be built from NAND
- Therefore every possible chip can be built from just the NAND gates!!!!



George Boole, 1815-1864
(*"A Calculus of Logic"*)


Boolean Function

- A Boolean function is a function that operates on binary inputs and return binary outputs
- Truth table is **every possible function evaluation** of the input variables
- [note 0 and 1 used to define false and true]
- Everything can be defined by a truth table

Composite Gates

$$f(A,B,C) = (A + B) \cdot \overline{C}$$

(A OR B) AND NOT C

 

A	B	C	$f(A,B,C)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Precedence

- Precedence

Parentheses evaluated first

Then **Not**

Then **And**

Then **Or**

Not X Or Y And Z = (Not X) Or (Y And Z)

Not X And Y Or Z = ((Not X) And Y) Or Z

Brackets over-rule everything...use when in doubt

((Not (X)) And (Y)) Or (Z)

Laws of Boolean Algebra

1. Law of Identity

$$A = A$$

$$\bar{A} = \bar{A}$$

2. Commutative Law

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

3. Associative Law

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(A + B) + C = A + B + C$$

4. Idempotent Law

$$A \cdot A = A$$

$$A + A = A$$

5. Double Negative Law

$$\bar{\bar{A}} = A$$

6. Complementary Law

$$A \cdot \bar{A} = 0$$

$$A + \bar{A} = 1$$

7. Law of Intersection

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$

8. Law of Union

$$A + 1 = 1$$

$$A + 0 = A$$

9. Distributive Law

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

10. Law of Absorption

$$A \cdot (A + B) = A$$

$$A + A \cdot B = A$$

11. Law of Common Identities

$$A \cdot (\bar{A} + B) = AB$$

$$A + (\bar{A} \cdot B) = A + B$$

12. De Morgan's Law

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

Simplify Boolean Expression

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$

$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(y)) =$

$\text{Not}(\text{Not}(x \text{ Or } y)) =$

double negation

$x \text{ Or } y$

Boolean Arithmetic

Binary to Decimal

- Each binary digit corresponds to a power of 2:

Place	7 th	6 th	5 th	4 th	3 rd	2 nd	1 st	0 th
Weight	2^7 = 128	2^6 = 64	2^5 = 32	2^4 = 16	2^3 = 8	2^2 = 4	2^1 = 2	2^0 = 1

- Where the digit is 1, we add the corresponding weight
- Example: convert $1100\ 1010_2$ into decimal

$$\begin{aligned}1100\ 1010_2 &= 1 \times 128 + 1 \times 64 + 0 \times 32 + 0 \times 16 \\&\quad + 1 \times 8 + 0 \times 4 + 1 \times 2 + 0 \times 1 \\&= 128 + 64 + 8 + 2 = 202_{10}\end{aligned}$$

Decimal to Binary

- Repeatedly divide by 2, until we reach 0
- The **right/left**-most binary digit is the **first/last** remainder
- E.g. $101_{10} = 1100101_2$

101	Remainder
50	1
25	0
12	1
6	0
3	0
1	1
0	1

- Example: convert 163_{10} into binary
- 10100011_2

Decimal to Binary (look-up table)

- $87 = 64$ ($64 = 2^6$, the biggest 2^n that 87 is divisible by) + 23 (remainder)
- $87 = 64 + 16$ ($16 = 2^4$, the biggest 2^n that 23 is divisible by) + 7 (remainder)
- $87 = 64 + 16 + 4$ ($4 = 2^2$, the biggest 2^n that 7 is divisible by) + 3 (remainder)
- $87 = 64 + 16 + 4 + 2$ ($2 = 2^1$, the biggest 2^n that 3 is divisible by) + 1 (remainder)
- $87 = 64 + 16 + 4 + 2 + 1$ ($1 = 2^0$, the biggest 2^n that 1 is divisible by) + 0 (remainder)
- Stop when remainder = 0

Representing Negative Numbers

- So far, unsigned numbers
 - How are negative numbers represented on a computer?
- What we use in decimal notation
 - $+/-$ and 0, 1, 2, \dots
- Such a representation is called **sign and magnitude**
- For binary numbers – define **leftmost** bit to be the **sign**
 - $0 \Rightarrow +$, $1 \Rightarrow -$
 - Rest of bits can be numerical value of number
 - Hence, only seven bits are left in a byte (apart from the sign bit), the magnitude can range from 0000000 (0) to 1111111 (127)
- Problems?

One's Complement

- Alternatively, a system known as **one's complement** can be used to represent negative numbers
- A negative binary number is the bitwise **NOT** applied to it — the "**complement**" of its positive counterpart
- E.g. the ones' complement form of 00101011 (43_{10}) becomes 11010100 (-43_{10})
- Still has two representations of 0: 00000000 (+0) and 11111111 (-0)
- The range of signed numbers using one's complement is represented by $-(2^{N-1} - 1)$ to $(2^{N-1} - 1)$ and ± 0
 - A conventional eight-bit byte is -127_{10} to $+127_{10}$ with zero being either 00000000 (+0) or 11111111 (-0)

Excess- n

- **Excess- n** , also called offset binary or biased representation, uses a pre-specified number n as a biasing value
- A value is represented by the unsigned number which is n greater than the intended value
- Therefore 0 is represented by n , and $-n$ is represented by the all-zeros bit pattern
- E.g. Excess-3
 - 0 is represented by 0011 (3)
 - +1 is represented by 0100 (4), +2 is represented by 0101(5)...
 - -1 is represented by 0010 (2), -2 is represented by 0001 (1)
 - -3 is represented by 0000 (0)

Two's Complement

- The **two's complement** of an N -bit binary number is defined as the complement with respect to 2^N
 - It is the result of subtracting the number from 2^N
 - $-x$ is represented as $2^N - x$
- There's a quicker way to calculate $2^N - x$:
 - $x + (1\text{'s complement of } x) = 2^N - 1$ (all 1 bits)
 - $2^N - x = (1\text{'s complement of } x) + 1$
 - Take the bitwise inverse (**NOT**) of x , then add 1 to result
- An N -bit two's-complement numeral system can represent every integer in the range $-(2^{N-1})$ to $+(2^{N-1} - 1)$
 - One's complement: $-(2^{N-1} - 1)$ to $(2^{N-1} - 1)$
- The sum of a number and its two's complement will always equal 0 (the last digit is ignored)
 - The sum of a number and its one's complement will always equal -0 (all 1 bits)

Example of 4-Bit Signed Encodings


Sign and Mag.		Ones' Comp.		Excess-3		Two's Comp.	
1111	-7	1000	-7	0000	-3	1000	-8
1110	-6	1001	-6	0001	-2	1001	-7
1101	-5	1010	-5	0010	-1	1010	-6
1100	-4	1011	-4	0011	0	1011	-5
1011	-3	1100	-3	0100	+1	1100	-4
1010	-2	1101	-2	0101	+2	1101	-3
1001	-1	1110	-1	0110	+3	1110	-2
1000	-0	1111	-0	0111	+4	1111	-1
0000	+0	0000	+0	1000	+5	0000	0
0001	+1	0001	+1	1001	+6	0001	+1
0010	+2	0010	+2	1010	+7	0010	+2
0011	+3	0011	+3	1011	+8	0011	+3
0100	+4	0100	+4	1100	+9	0100	+4
0101	+5	0101	+5	1101	+10	0101	+5
0110	+6	0110	+6	1110	+11	0110	+6
0111	+7	0111	+7	1111	+12	0111	+7

Adder

- Build an Adder:
 - Half adder: adds two bits
 - Full adder: adds three bits
 - Adder: adds two integers

Half Adder

 - Add **two** single binary digits and provide the **output** plus a **carry value**
- It has two inputs, called A(a) and B(b), and two outputs S (sum) and C (carry)



Half Adder

- Least significant bit in the addition is called sum ($a+b$)
- Most significant bit is called carry (carry of $a+b$)


a	b	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- **Never has a situation when sum and carry are both 1**

Half Adder


a	b	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 - The common representation uses a XOR and a AND gate



Full Adder

 - Add **three** single binary digits and provide the **output** plus a **carry value**
- It has three inputs, called A, B and Carry(in), and two outputs S (sum) and Carry(out)




Full Adder

- Least significant bit in the addition is called sum ($a+b+c_{in}$)
- Most significant bit is called carry(out) (carry of $a+b+c_{in}$)

a	b	Carry(in)	Carry(out)	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder: Implementation

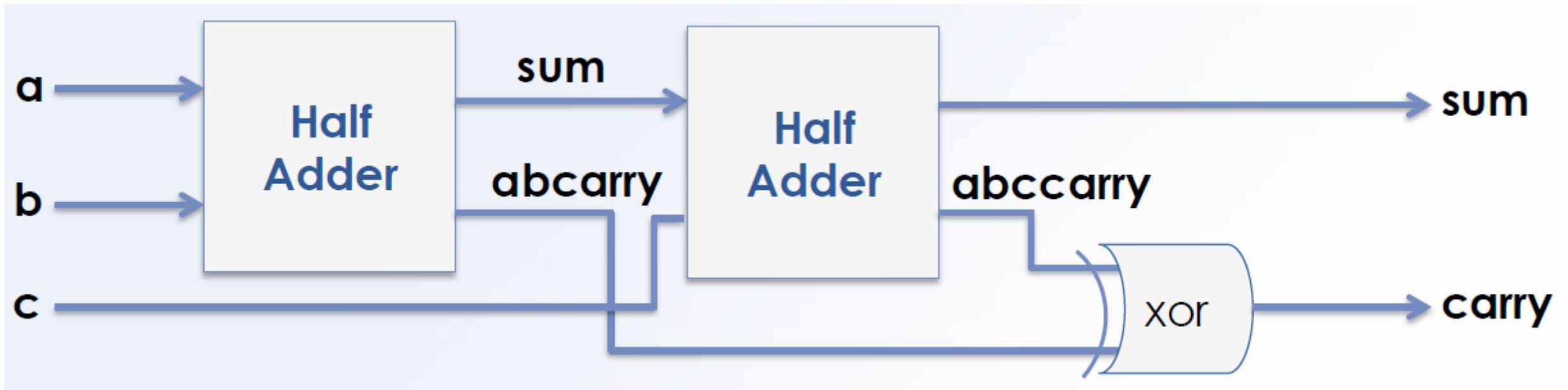- Use two half adders to build a full adder



A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


Sequential Logic and ALU

Sequential Logic Circuits

- Combinational chips compute functions that **depend solely on combinations of their input values**
- Sequential Logic Circuits
 - Output depends **not only on the present value** of its input signals but **on the sequence of past inputs**, the input history as well


Flip Flops

 - The flip flop is the most elementary sequential element in the computer
- Data Flip Flop (DFF): the simplest state keeping gate (built-in)



- Contains a **single** bit **input** and a **single** bit **output**


Flip Flops

 

- The gate outputs its previous input: $out(t) = in(t-1)$
- Implementation: a gate that can flip between two stable states:
 - Remembering 0/Remembering 1
 - Also can be made from looping NAND gates

Register

 
- A register is a storage device that can “**store**” or “**remember**” a value over time
- Typically is composed of flip flops
- 1-bit register:
 - Store (maintain) a bit
 - Until it is instructed to load(store) another bit



if $\text{load}(t)$ then $\text{out}(t+1) = \text{in}(t)$
else $\text{out}(t+1) = \text{out}(t)$

1-bit Register: Implementation

 - The select bit of the Mux can become the load bit!




Arithmetic Logical Unit

- **A combinational circuit** that performs arithmetic and bitwise operations on integers represented as binary numbers.
- Input the **data** and some **code for the operation**
- Output will be some **data** and any **additional information**
- ALUs perform simple functions, because of this they can be executed at high speeds (i.e., very short propagation delays)

The Arithmetic Logical Unit

The ALU computes a function on the two inputs, and outputs the result

 f : one out of a family of pre-defined arithmetic and logical functions




- Arithmetic functions: integer addition, multiplication, division, ...
- logical functions: And, Or, Xor, ...

Which functions should the ALU perform?
A hardware / software tradeoff.

The Hack ALU

 
- Operates on two 16-bit, two's complement values
- Outputs a 16-bit, two's complement value
- Which function to compute is set by six 1-bit inputs
- Computes one out of a family of 18 functions
- Also outputs two 1-bit values
 - if the ALU output is 0, zr is set to 1; otherwise zr is set to 0
 - If $\text{out} < 0$, ng is set to 1; otherwise ng is set to 0



out
0
1
-1
x
y
!x
!y
-x
-y
x+1
y+1
x-1
y-1
x+y
x-y
y-x
x&y
x y

The Hack ALU

 To cause the ALU to compute a function, set the control bits to one of the binary combinations listed in the table.



control bits

zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Memory

Fetch-Decode-Execute Cycle

- At some level, every programmable processor implements a **fetch-execute cycle**
- Automatically implemented by processor hardware, allows processor to move through program steps
- **Fetch** — The opcode for the instruction is fetched from memory
- **Decode** — Opcode decoded to work what parts of the CPU are needed
- **Execute** — CPU processes the instruction
- And repeat for the next instruction

Fetch-Execute Algorithm

Repeat {

Fetch (PC) :

- Fetch the instruction word (at PC)
- Instruction decoded
- Calculate next instruction address


Execute (ALU, Registers and Control) :

- Read operands
- Executes the operations
- Write/store results

}

Memory Hierarchy

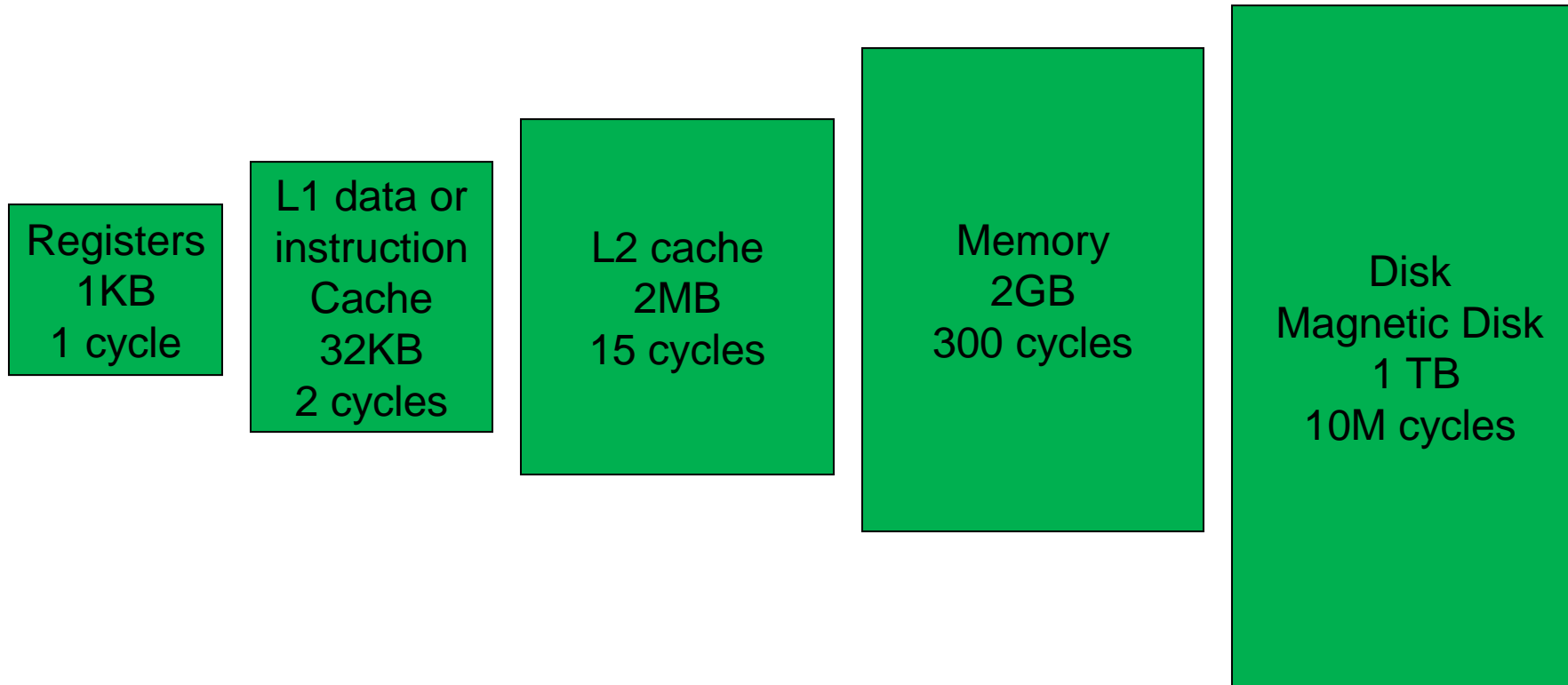- As it goes further, capacity and latency increase



The Hack Computer: Main Parts

- Instruction memory (ROM)
- Memory (RAM)
 - Data memory
 - Screen (memory map)
 - Keyboard (memory map)
- CPU
- Computer (the logic that holds everything together)

The Hack Computer (Put Together)

