



**University of  
Nottingham**

UK | CHINA | MALAYSIA

# Digital Blocks and ALU Design

Dr. Heng Yu

AY2022-23, Spring Semester  
COMP1047: Systems and Architecture  
Week 5



## Today's outline

- ✓ Basic digital building blocks
  - Gates, Arithmetic circuits, multiplexers, registers
- ✓ Constructing an arithmetic logic unit
  - Add, sub, and, or, nor
  - Set-on-less-than






# Learning Objectives

- Recap on basic digital circuit components
- Understand the function and control of a MIPS ALU
- Design a MIPS ALU with given arithmetic operations


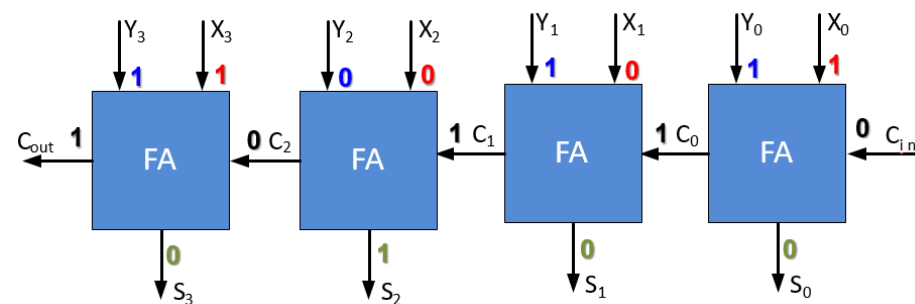  
## Introduction


- Digital building blocks include:
  - ➔ Gates, arithmetic circuits, multiplexers, decoders, registers, counters, memory arrays, logic arrays, etc.
- Building blocks are important in their own right and they demonstrate hierarchy, modularity, and regularity:
  - ➔ They are built from a hierarchy of simpler components.
  - ➔ They have well-defined interfaces and functions.
  - ➔ Their regular structure is easily extended to different sizes.
- We'll use many of these building blocks to build a microprocessor in subsequent weeks.



Digital Building Blocks

1-bit adders


Half Addder

 

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Addder

 

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

# Multi-bit adders

- Also called carry propagate adder (CPA). Several types of design available:
  - ★ Ripple carry adder (slow)
  - ★ Carry-Lookahead adder
  - ★ Prefix adder
- Faster adders require more hardware.

## Ripple carry adder


- Chain 1-bit adders together
- Disadvantage: **slow**
- The delay of an  $N$ -bit ripple-carry adder is:

$$t_{\text{ripple}} = Nt_{FA}$$


where  $t_{FA}$  is the delay of a full adder

Think about it:

Illustrate the process that a RCA works.

 

General symbol of a multi-bit adder.

 


A 32-bit ripple carry adder.


## Subtractor

- $-B = B' + 1$  (2's complement representation)
- $A - B = A + B' + 1$  (use CPA where  $C_{in} = 1$ )
- Bit-wise inverse of B is  $B'$

### Symbol

 


### Implementation

 


# Comparator: Equality


## Symbol

 

## Implementation

 

## XNOR

 


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1



 
## Comparator: Less than

- Calculate  $A - B$ . If  $A < B$ , then result is negative  $\Rightarrow$  2's complement numbers, (N-1)th bit is 1.


 
# Multiplexer

- Selects between **one** of  $N$  inputs to connect to the output.
- $\log_2 N$ -bit input selection



$S$	$D_1$	$D_0$	$Y$	$S$	$Y$
0	0	0	0	0	$D_0$
0	0	1	1	1	$D_1$
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		



Think about it:

for 4-input mux, how many  $S$  bits are required? How about 8, 16, 32, ...

A 2-to-1 multiplexer
  
## Register

- Register: stores data in a circuit
- Uses a clock signal to determine when to update the stored value
- Edge-triggered: update when Clk changes from 0 to 1 (rising edge)
- Synchronous circuit



## Today's outline

- ✓ Basic digital building blocks
  - Gates, Arithmetic circuits, multiplexers, registers
- ✓ Constructing an arithmetic logic unit
  - Add, sub, and, or, nor
  - Set-on-less-than

Define our ISA first!

Let's use a *subset* of the MIPS instructions.

✓ R-Type:

- ★ `add rd, rs, rt`
- ★ `sub rd, rs, rt`
- ★ `and rd, rs, rt`
- ★ `or rd, rs, rt`
- ★ `slt rd, rs, rt`

✓ Load/Store:




- ★ `lw rt,rs,imm16`
- ★ `sw rt,rs,imm16`

✓ Imm operand:

- ★ `addi rt,rs,imm16`

✓ Branch:

- ★ `beq rs,rt,imm16`

   

Define our ISA first!

Let's use a *subset* of the MIPS instructions.

✓ R-Type:

- ★ `add rd, rs, rt`
- ★ `sub rd, rs, rt`
- ★ `and rd, rs, rt`
- ★ `or rd, rs, rt`
- ★ `slt rd, rs, rt`

✓ Load/Store:

- ★ `lw rt,rs,imm16`
- ★ `sw rt,rs,imm16`


✓ Imm operand:

- ★ `addi rt,rs,imm16`

✓ Branch:

- ★ `beq rs,rt,imm16`

 What are the common  
operations involved in  
those instructions?



Requirements: must support the following arithmetic and logic operations

**add, sub**: two's complement adder/subtractor

**and, or** : logical AND, logical OR


**slt** (set on less than): two's complement adder with inverter, check sign bit of result



## Functional specification

Remember the operations needed:

**add, sub, and, or, slt**

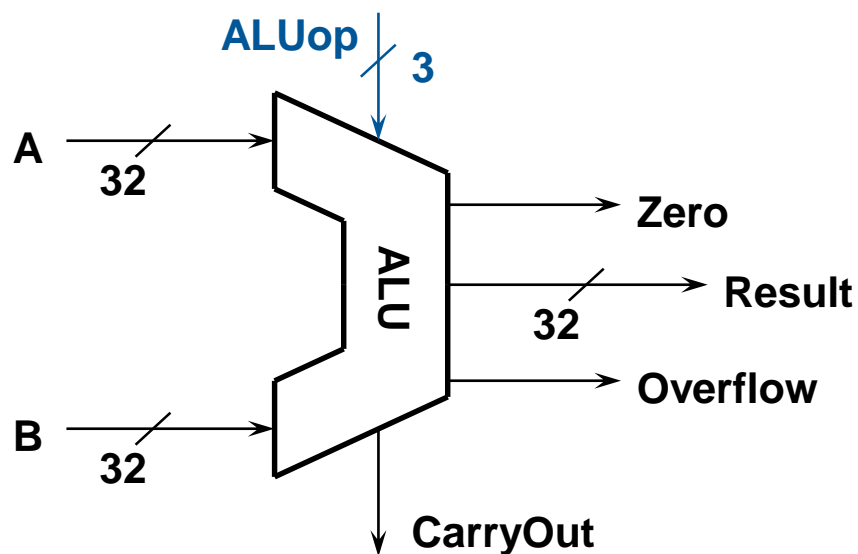

<u>ALU Control (ALUop)</u>	<u>Operation</u>
000	and
001	or
010	add
110	subtract
111	set-less-than





**Why ALUop needs 3 bits?**

## A bit-slice ALU
 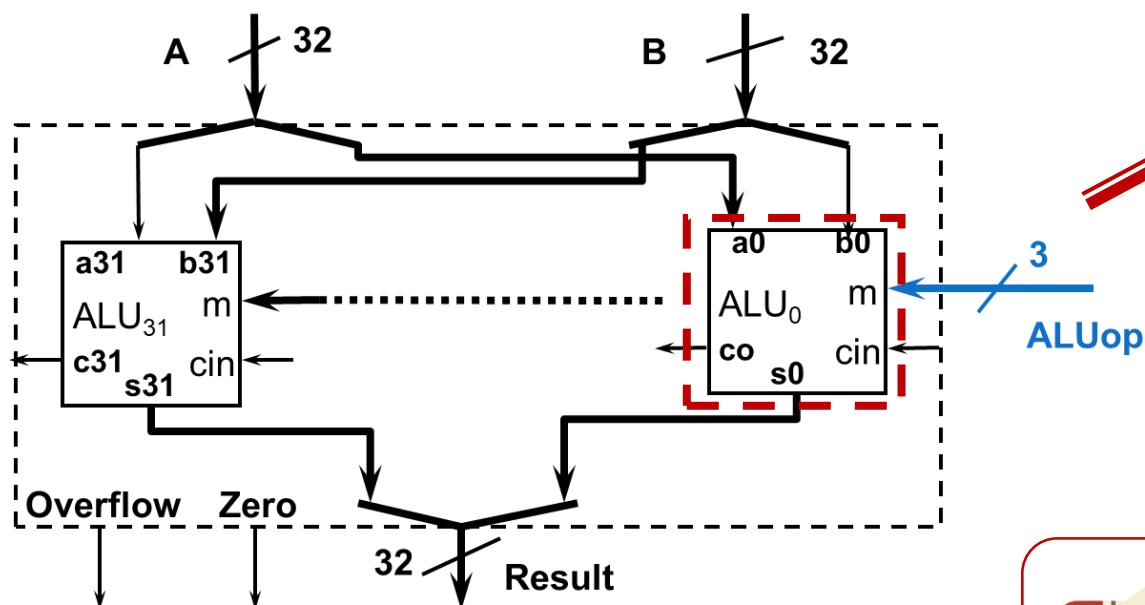
### ➔ Design trick 1: **divide and conquer**


- Break the problem (32-bit ALU) into simpler problems (1-bit ALU), solve them and glue together the solution.



Note that the 'overflow' and 'zero' signals are not shown in this material, for simplicity. Basically, you need to design additional and specific circuits to output them. Take them as exercises with you.
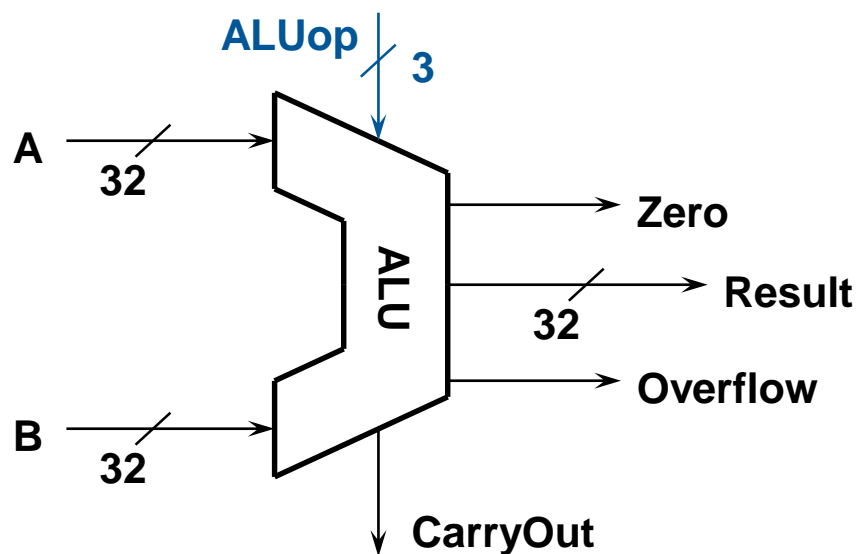
## A bit-slice ALU

- ➔ Design trick 2: [Work on what you already have](#)
- Solve part of the problem and extend based on it.
  - E.g., realize the 'and', 'or', and 'add' functionalities, then extend to 'sub', and 'slt'.



<u>ALU Control (ALUOp)</u>	<u>Operation</u>
000	and
001	or
010	add
110	subtract
111	set-less-than



## Designing the ALU

- Let's make a pre-design analysis.
- What are the digital building blocks really needed to realize the five operations ('and', 'or', 'add', 'sub', and 'slt')?
  - One **AND** gate, one **OR** gate, and one **ADDER**.
  - 'sub' can be done by the **ADDER**.
  - 'slt' needs to subtract, so it can also be done by the **ADDER**.
  - One **multiplexer** for the ALUop control signal to select and output one result from the multiple incoming results (namely, from AND, OR, ADDER)
  - Maybe more.


<u>ALU Control (ALUop)</u>	<u>Operation</u>
000	and
001	or
010	add
110	subtract
111	set-less-than

## Designing the ALU

- Let's design the 'slt' functionality.
- What does 'slt' do, and what does it output?
  - Firstly, 'slt Y, x1, x2' firstly subtracts x2 from x1 (i.e.,  $x1 - x2$ )
  - Then, it should compare the result with zero.
    - If  $x1 - x2 < 0$ , then Y is set ( $Y = 1$ )
    - Else, then  $Y = 0$ .
  - Given Y being 32-bit binary
    - If  $x1 - x2 < 0$ , then Y is set ( $Y = 0000 \dots 0001$ )
    - Else, then  $Y = 0000 \dots 0000$ .

But how to make  $Y = 1$  when  $x1 - x2 < 0$ ?

 
- In 2's complement format, the result of  $x1 - x2$  is  $1xxx \dots xxxx$ , if  $x1 - x2 < 0$ . Only need to shift the leading digit back, from position 31 to position 0. This is how Y is obtained.



'slt' is a 'sub', but needs special attendance.



## The ALU Design

 


$F_{2:0}$	Function
000	A & B
001	A   B
010	A + B
110	A - B
111	SLT



One particular suggestion:

 - ✓ Digital design and computer architecture, 1<sup>st</sup> or 2<sup>nd</sup> ed; by D. Harris & S. Harris
- ✓ Available in UNNC library ([link](#))
- ✓ A simplified version of the Patterson & Hennessey Book.
- ✓ An ARM RISC ISA version also available in library.





University of  
**Nottingham**

UK | CHINA | MALAYSIA

**Thank you.**