

COMP1036 Computer Fundamentals

Lab 2

You are required to implement the following logic circuits using only NAND gate and any other gates you have previously implemented. Therefore, you need to implement the circuits in the **following order**:

1. NOT
2. AND
3. OR
4. XOR
5. Mux
6. DMux
7. Not16

16-bit Not gate: for i = 0..15: out[i] = Not in[i]

8. And16

16-bit-wise And gate: for i = 0..15: out[i] = a[i] And b[i]

9. Or16

16-bit bitwise Or gate: for i = 0..15 out[i] = a[i] Or b[i]

10. Mux16

16-bit multiplexor. If sel == 1 then out = b else out = a

11. Or8Way

8-way Or gate: out = in[0] Or in[1] Or ... Or in[7]

12. Mux4Way16

4-way 16-bit multiplexor.
out = a if sel == 00
out = b if sel == 01
out = c if sel == 10
out = d if sel == 11

13. Mux8Way16

```
8-way 16-bit multiplexor.  
out = a if sel == 000  
out = b if sel == 001  
out = c if sel == 010  
out = d if sel == 011  
out = e if sel == 100  
out = f if sel == 101  
out = g if sel == 110  
out = h if sel == 111
```

14. DMux4Way

```
4-way demultiplexor.  
{a,b,c,d} = {in,0,0,0} if sel == 00  
{a,b,c,d} = {0,in,0,0} if sel == 01  
{a,b,c,d} = {0,0,in,0} if sel == 10  
{a,b,c,d} = {0,0,0,in} if sel == 11
```

15. DMux8Way

```
8-way demultiplexor.  
{a,b,c,d,e,f,g,h} = {in,0,0,0,0,0,0,0} if sel == 000  
{a,b,c,d,e,f,g,h} = {0,in,0,0,0,0,0,0} if sel == 001  
{a,b,c,d,e,f,g,h} = {0,0,in,0,0,0,0,0} if sel == 010  
{a,b,c,d,e,f,g,h} = {0,0,0,in,0,0,0,0} if sel == 011  
{a,b,c,d,e,f,g,h} = {0,0,0,0,in,0,0,0} if sel == 100  
{a,b,c,d,e,f,g,h} = {0,0,0,0,0,in,0,0} if sel == 101  
{a,b,c,d,e,f,g,h} = {0,0,0,0,0,0,in,0} if sel == 110  
{a,b,c,d,e,f,g,h} = {0,0,0,0,0,0,0,in} if sel == 111
```